

**Circuits**  
Practice Problem

1. Find all the unmarked values.

